

Digital Electronics Lab Report

Submitted by : Neelesh Dorairaj

Roll number : 24EE10015

Lab code : EE29210

Date of experiment : 27-1-26

Experiment 3: IC-74181, 4-bit ALU

Objectives:

Verify all 16 arithmetic and 16 logical operations on two 4-bit words, and see the output on a 7-segment LED display or series of bi-coloured LEDs.

Apparatus:

1. IC-74181
2. LED Bar
3. Resistor 470 or 390 - 8
4. Resistor 1k-14
5. Breadboard
6. DIP switches with 4 or more switches-2
7. Connecting wires

8. DC power supply

Theory:

An Arithmetic Logic Unit (ALU) is the core computational block of a digital system. It performs:

1. Arithmetic operations - addition, subtraction, increment, decrement, etc.
2. Logical operations - AND, OR, XOR, NOT, etc.


The IC-74181 is one of the most popular ALUs, capable of performing 32 operations on two 4-bit inputs.

Operates on two 4-bit inputs $A_3A_2A_1A_0$, $B_3B_2B_1B_0$ and produces a 4-bit output $F_3F_2F_1F_0$

Function Select Inputs S_0-S_3 are the four pins which select which operation is performed. Total combinations = $2^4 = 16$. Each combination corresponds to a unique operation. Carry input is used only for arithmetic and allows addition with carry and subtraction.

The IC-74181 successfully performs 32 distinct operations (16 arithmetic + 16 logic) on 4-bit binary inputs using control signals. By varying M , S_0-S_3 , and C_n , we can verify all operations practically, proving the working of a basic ALU.

Circuit Diagram:

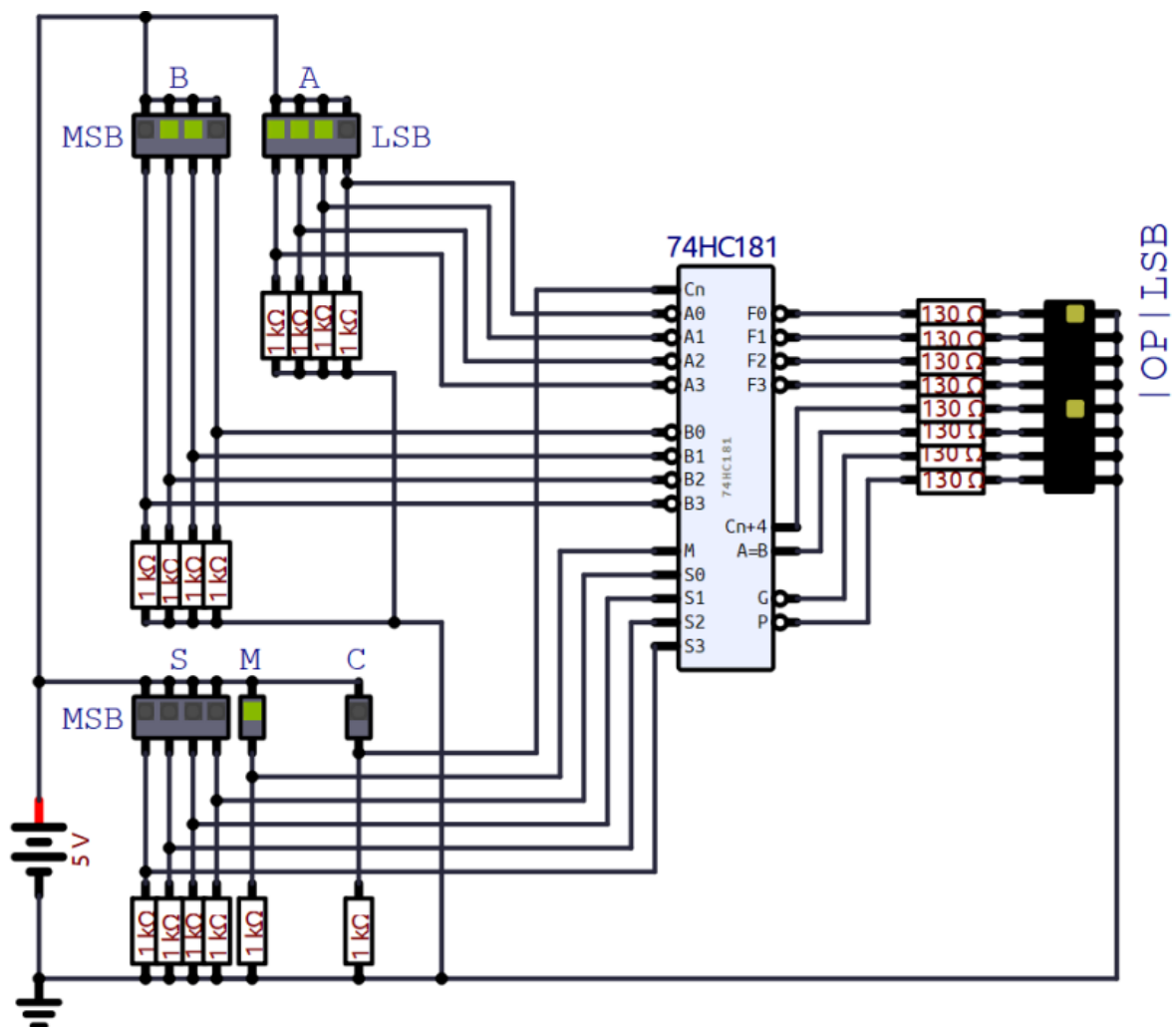


The operands A and B are applied to the ALU. Depending on mode M and function select inputs S_0 – S_3 , either the arithmetic or logic unit is enabled. The computed result appears at F_0 – F_3 , while carry and comparison outputs indicate overflow and equality. M is for selecting the mode $M=0$ is for arithmetic and $M=1$ is for logical


Output/Observation:

Logical : $M=H$, For all cases $A=0101$, $B=1001$


1. LLHH

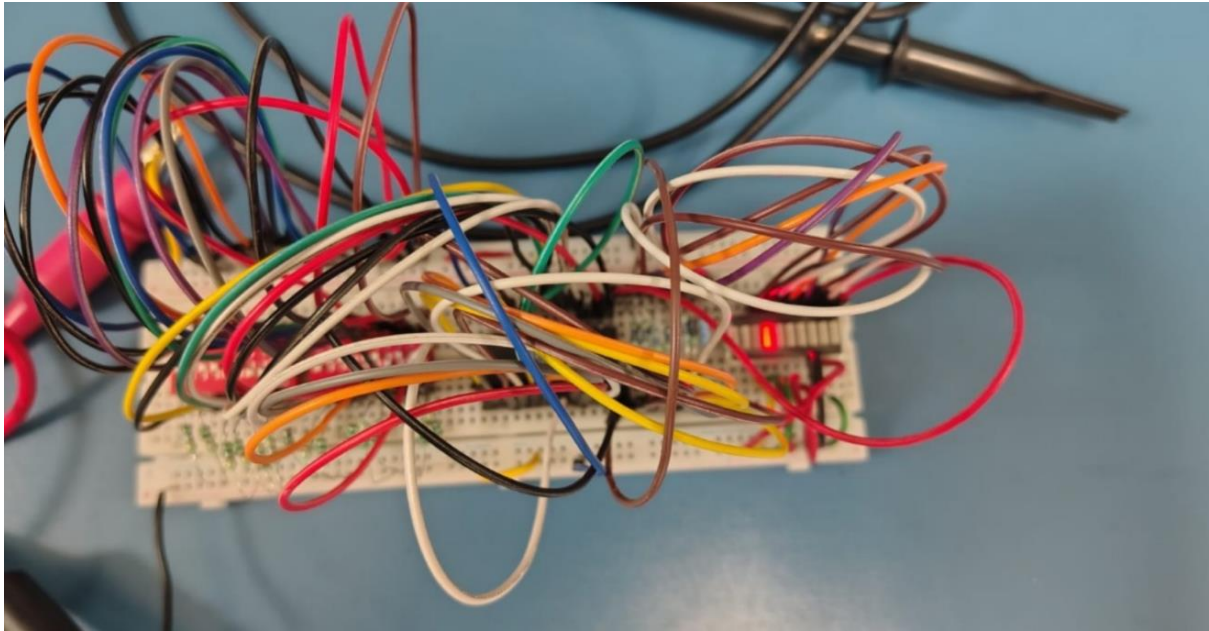

2. HLHL

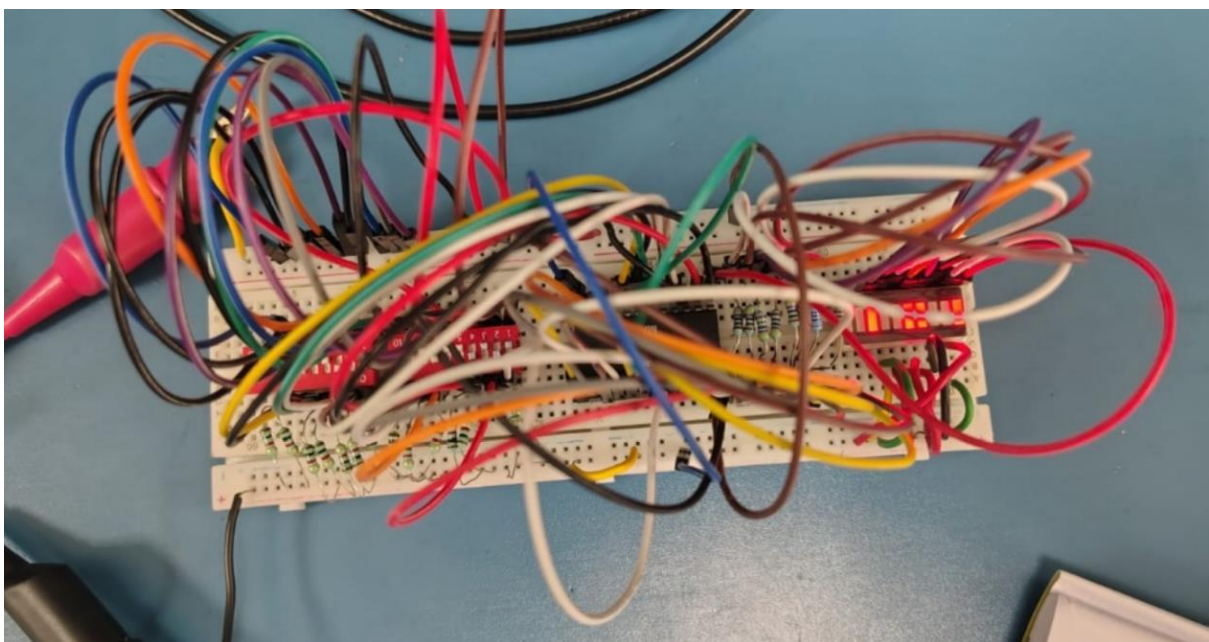


3. HHHH

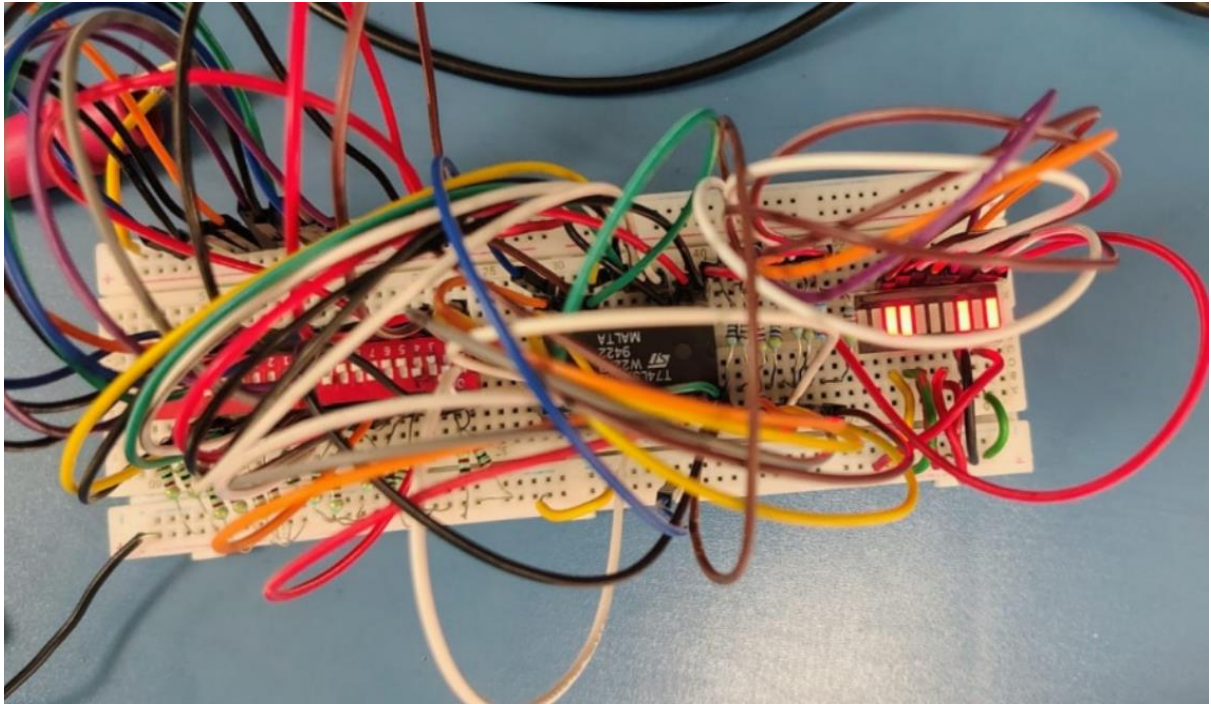


Arithmetic : $M=L$, $C_n=L$


1. LLLL

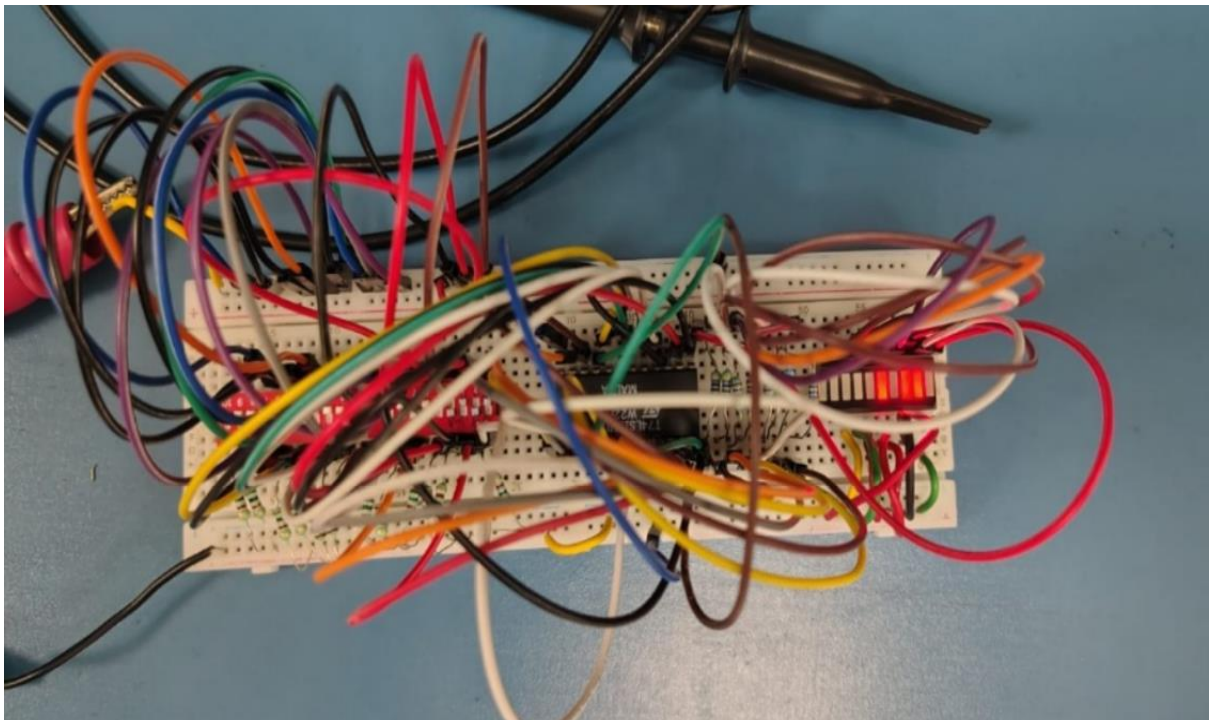

2. HHLH

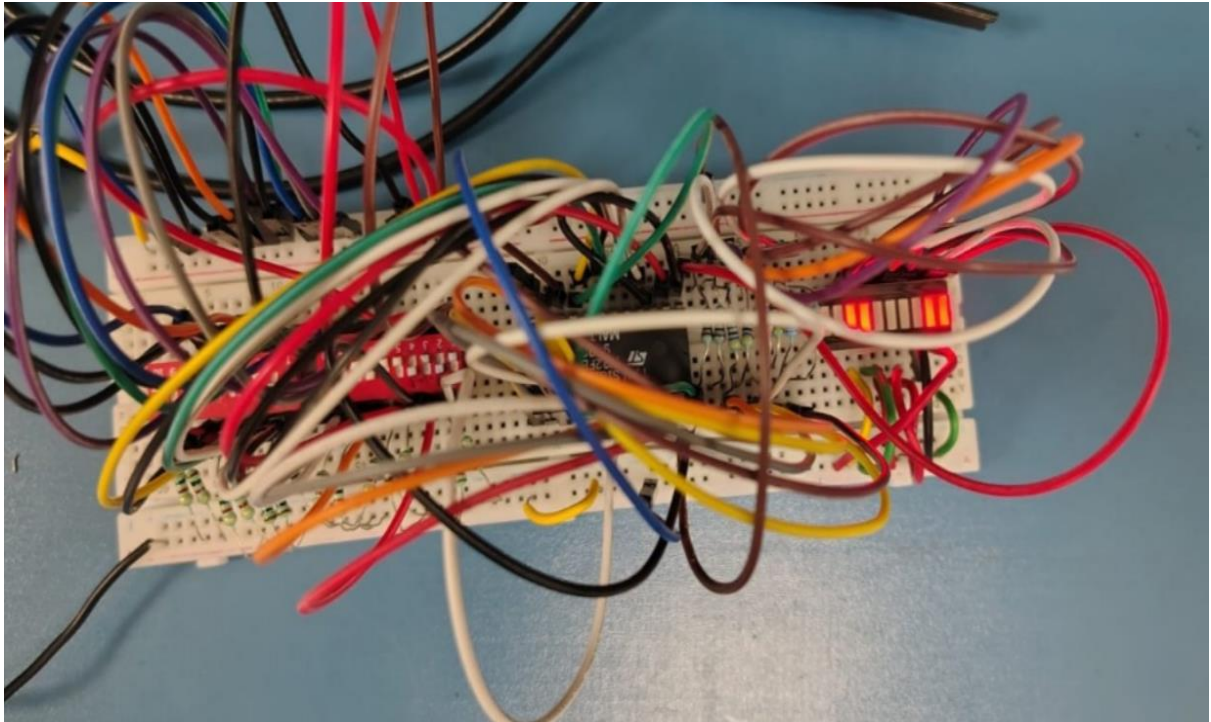


3. HLLH

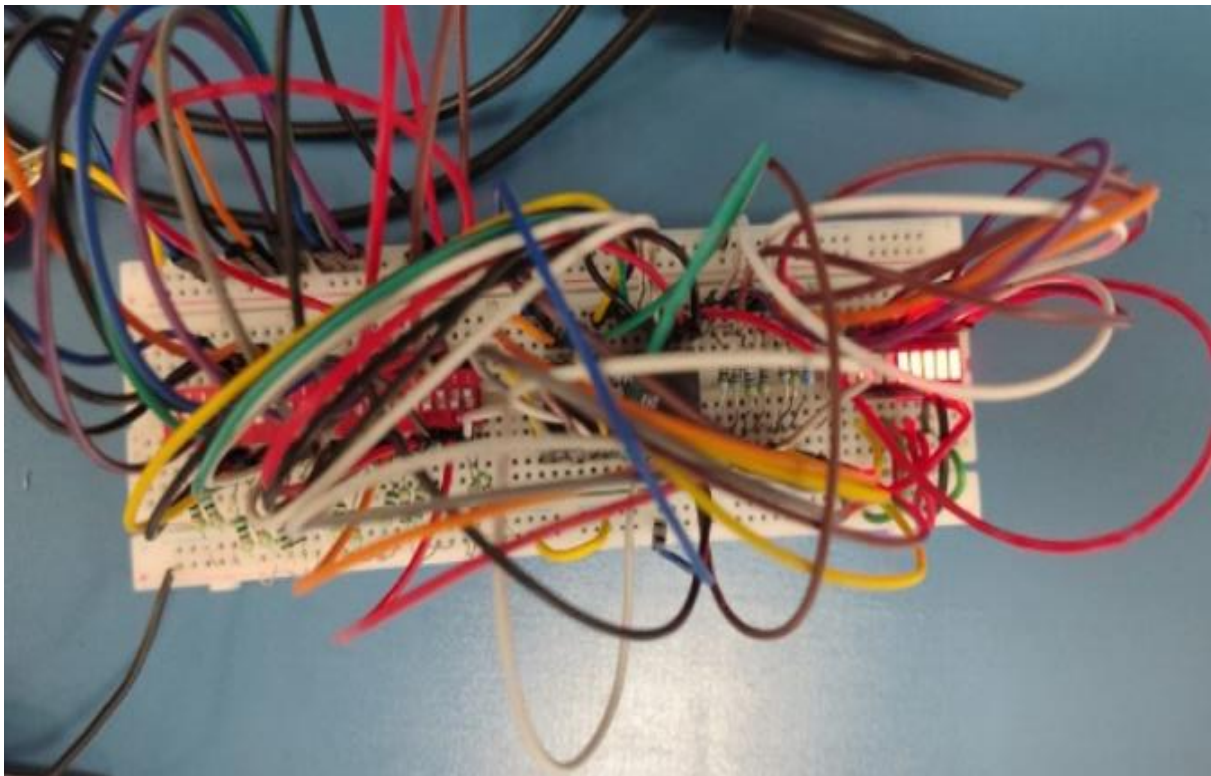


Arithmetic : $M=L$, $C_n=H$


1. HLLH

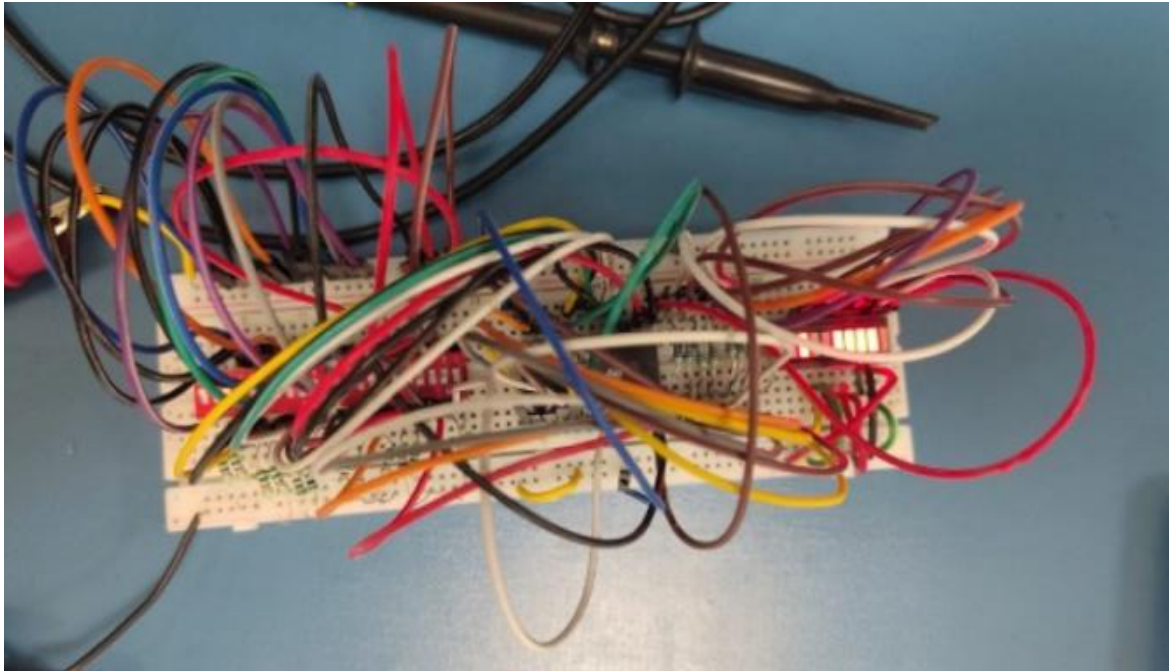

2. LHHL

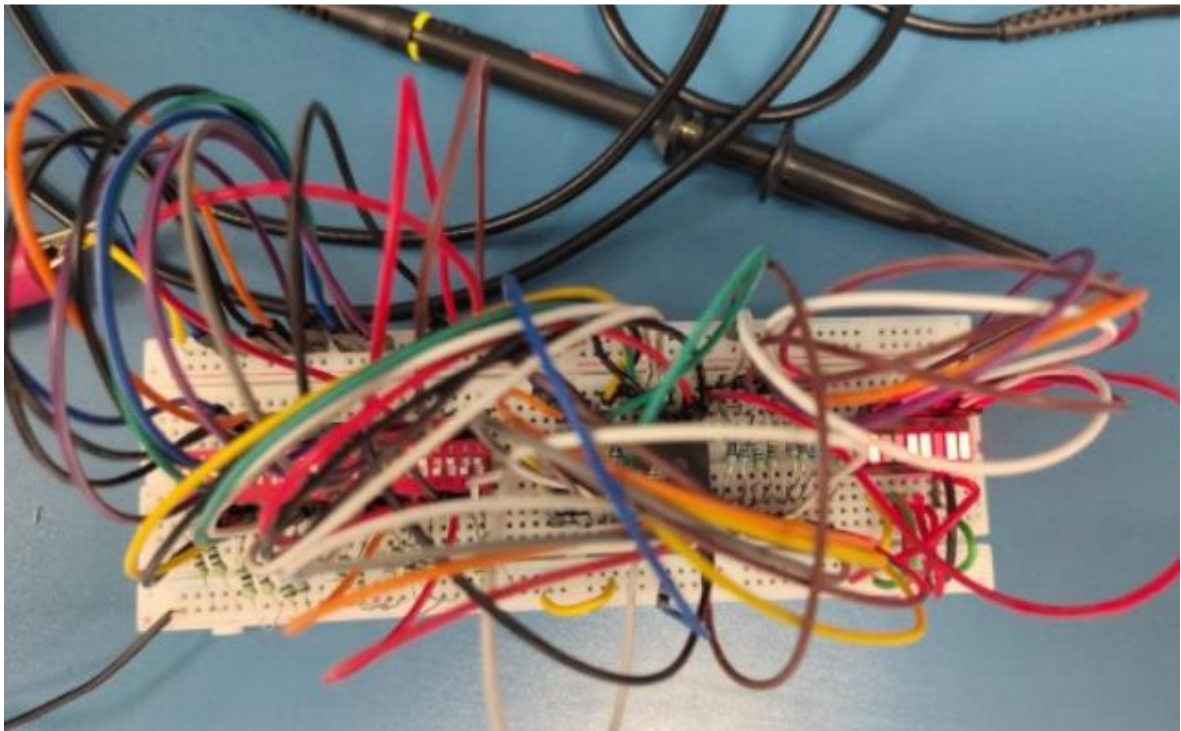

3. HLHH

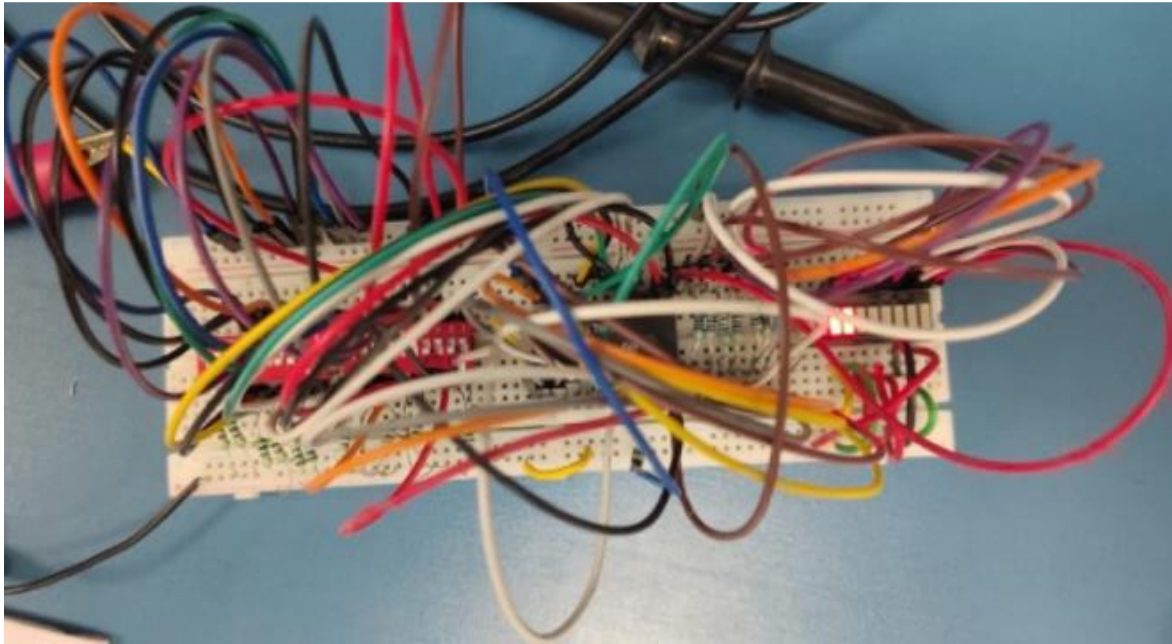

Conclusion:

The IC-74181 (4-bit ALU) was successfully tested and its operation verified. For different select input combinations (S_3 – S_0):

Arithmetic mode ($M = 0$) was verified for both cases of carry input ($C_n = 0$ and $C_n = 1$). Logic mode ($M = 1$) was verified for the corresponding select inputs. The behaviour under active-high and active-low logic conditions was also verified.

For all test cases, the 4-bit output (F_3 – F_0) matched the expected values from the 74181 function table, confirming correct arithmetic and logical operation.